

# POWER ELECTRONICS [ELE 603]

1- Books to be referred:


- a) Power Electronics: Converters, applications and design by Mohan, Undeland and Robbins.
- b) Daniel Hart
- c) M.H. Rashid
- d) Issah Batterseh.
- e) Lecture Notes / NPTEL.

# LECTURE - I

\* What is power electronics?

The control of power through electronics :

e.g.

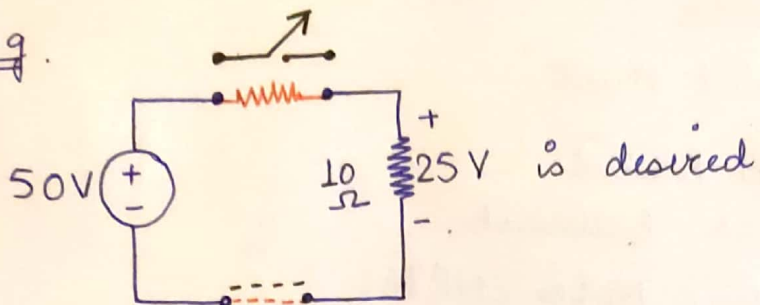

Soln(1)  $\Rightarrow$  Using a resistance  $= 10 \Omega$  to drop 25V in series

Problem  $\Rightarrow$  Efficiency is 50%.

$\Rightarrow$  losses in resistor.


$\Rightarrow$  No control (dynamic) over  $V_o$ .

Sol<sup>n</sup> (2)  $\Rightarrow$  Using a switch in series with the load-source arrangement.

Assuming this switch to be ideal  $\Rightarrow$

When 'S' is ON  $\Rightarrow V_o = 50V$ .

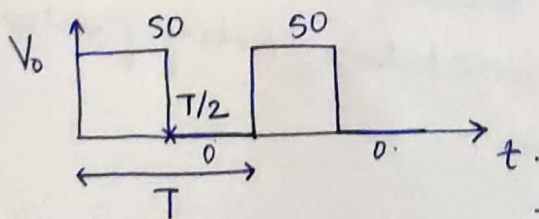When 'S' is OFF  $\Rightarrow V_o = 0V$ .



$$V_{o,avg} = \frac{1}{T} \int_0^T v_o(t) dt = \frac{1}{T} \int_0^{T/2} 50 dt = \frac{50 \times T}{T \times 2} = \underline{\underline{25V}}$$

Advantage: Assuming this switch is ideal.  
\* efficiency  $\approx 100\%$ .

\* To Summarize:  $\rightarrow$ .

"The use of electronic switches (devices) to control power is the basis of power electronics".

Why electronic switch instead of a mechanical switch?

- i) Fast response. ( $\mu\text{s}$  versus  $\text{secs}$ ).
- ii) Very less losses.

\* Now using electronic switches, how can I control power:  $\rightarrow$ .

- 1) AC-DC { 230V, 50Hz, 1- $\phi$  AC to fixed/variable DC }
- 2) DC-DC { fixed DC to variable DC  
 $\hookrightarrow$  step-up/step-down.  
 $\hookrightarrow$   $\hat{c}$ out transformer }
- OR.  
{ variable DC to fixed DC }
- 3) DC-AC { Inverters/UPS }  
fixed DC to AC ( $V$ ,  $f$ ).
- 4) AC-AC { voltage/frequency control }




# ELECTRONIC SWITCHES / DEVICES.

"At power level"

A power electronic device is characterised by 2 features:-

- VBC (1) Voltage blocking capability (at 0 current)
- CCC (2) Current carrying capability (at 0 voltage drop)

Coming back to the same ckt:-

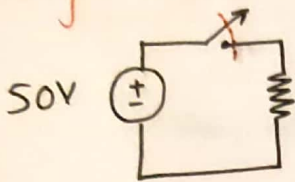


Ratings are decided as per VBC/CCC



- ON (closed)
  - carrying current (drop is zero) } CCC
- OFF (OPEN)
  - current is zero.
  - { 50V across switch } blocking it VBC

## DEVICE CHARACTERISTICS

1) Diode (Power)  
Uncontrolled

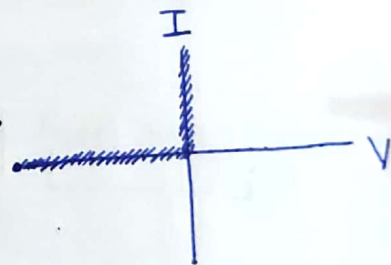

2) Thyristor (SCR)


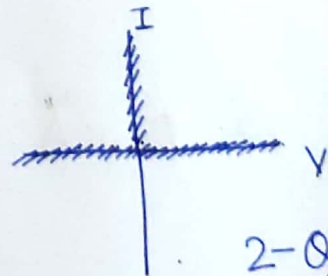
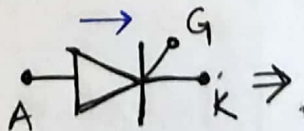


- Semi-Controlled
- Current controlled
- $V_{AK} = +ve$ 
  - Forward Bias.
  - does not conduct till gate is high.
- $V_{AK} = -ve$ 
  - reverse bias
  - OFF
  - irrespective of gate
  - Diode like behaviour.


IGBT/MOSFET. Similar behaviours  
 $f_s \uparrow \rightarrow$  MOSFET, Ratings  $\uparrow \rightarrow$  IGBT.

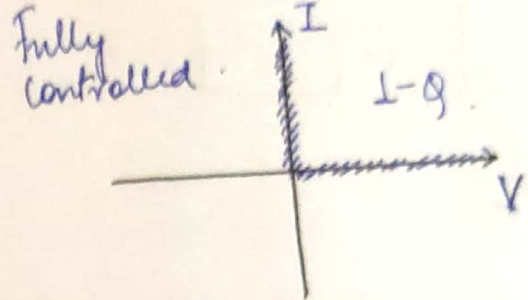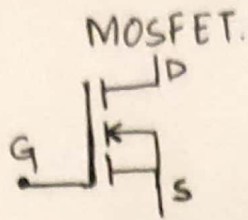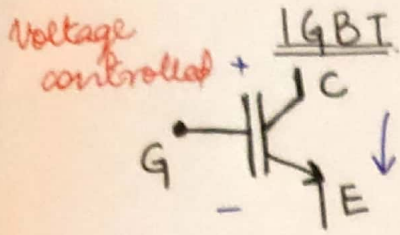3) IGBT (Insulated Gate Bipolar Transistor)





Power MOSFET (Metal-Oxide Field Effect Transistor)



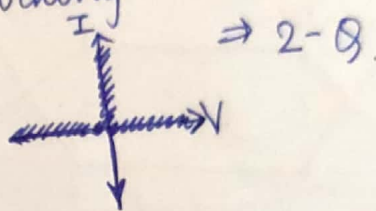
Special type of IGBT.  
 called reverse blocking  
 IGBT.



Developing a 4-Q switch

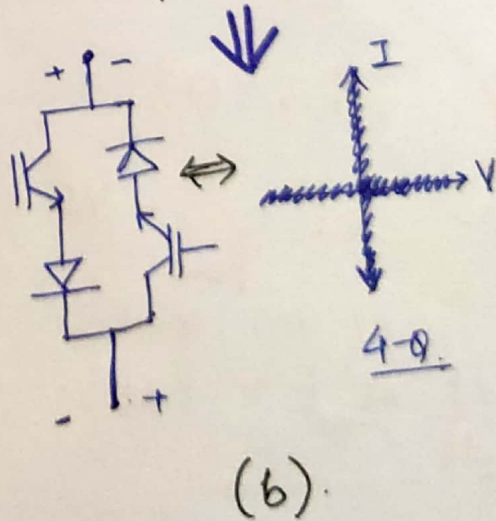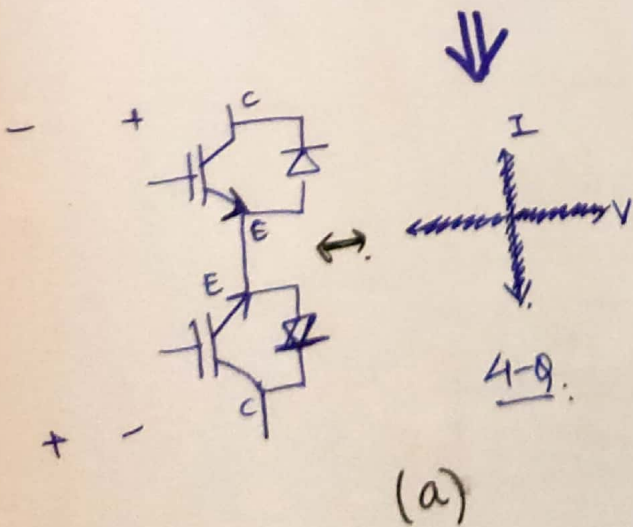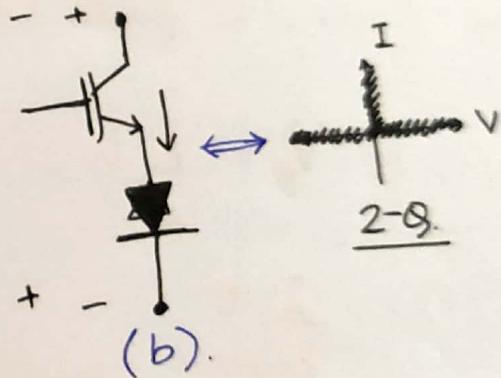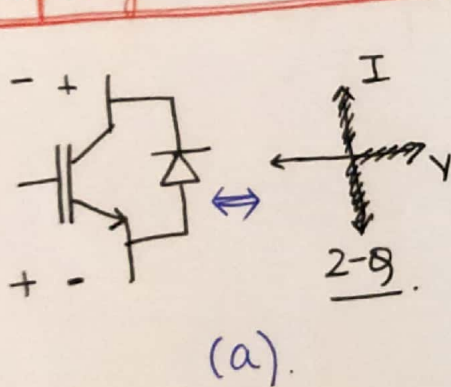


# Ideal Switch Behaviour [LECTURE 2]

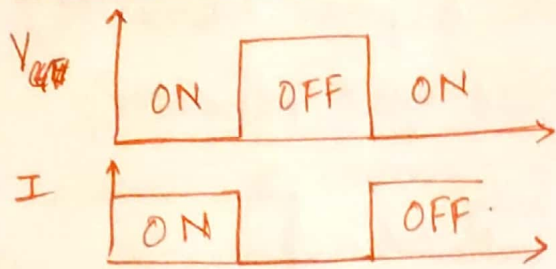

$$P_{\text{loss}} = 0.$$

# Practical Switch Behaviour

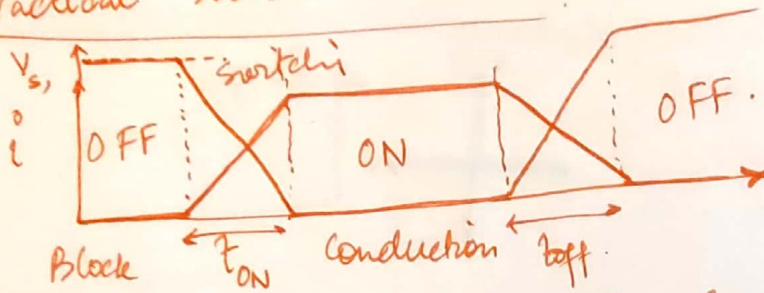

Loss. ( $v \times i$  is finite) during  $t_{\text{on}}$  &  $t_{\text{off}}$ .

$$v(t) = V_0 - \frac{V}{t_{\text{on}}} t.$$

$$i(t) = \frac{I}{t_{\text{on}}} t.$$

$$P = v(t) \times i(t)$$

$$= VI \frac{t}{t_{\text{on}}} - VI \frac{t^2}{t_{\text{on}}^2}.$$

$$P = \frac{dE}{dt} \Rightarrow E = \int_0^{t_{\text{on}}} P dt = \frac{VI}{t_{\text{on}}} \frac{t_{\text{on}}^2}{2} - \frac{VI}{t_{\text{on}}^3} \frac{t_{\text{on}}^3}{3}$$

$$\underline{\text{Energy loss.}} = \frac{VI}{6} \left[ t_{\text{on}} \right].$$



During  $t_{off}$  :-

$$v(t) = \frac{V}{t_{off}} \times t, \quad i(t) = I - \frac{I}{t_{off}} \times t$$

$$P = v(t) \times i(t) = VI \frac{t}{t_{off}} - VI \frac{t^2}{t_{off}^2}$$

$$E = \int_0^{t_{off}} P dt = \frac{VI t_{off}}{2} - \frac{VI t_{off}}{3}$$

$$\text{Energy loss} = \frac{VI}{6} \{t_{off}\}$$

$$\text{Net loss of Energy} = \frac{1}{6} VI \{t_{on} + t_{off}\}$$


$$P = \frac{dE}{dt} = \frac{VI}{6 T_s} \{t_{on} + t_{off}\}$$

$$P = \frac{VI}{6} \times f_s \{t_{on} + t_{off}\}$$


$V, I \Rightarrow$  depend on circuit conditions.

$t_{on}/t_{off} \Rightarrow$  device specifics (data-sheet)
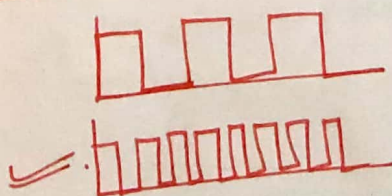
$$t_{on}/t_{off} \downarrow \Rightarrow f_s \uparrow$$



$f_s \uparrow$   
\* desired

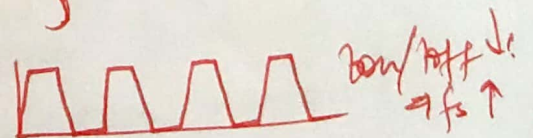

$t_{on}/t_{off} \downarrow \Rightarrow f_s \uparrow$   
 $t_{on}/t_{off} \uparrow \Rightarrow f_s \downarrow$


Power MOSFET  $\Rightarrow t_{on}/t_{off} \downarrow \Rightarrow f_s \uparrow \approx 100-200$  KHz.

IGBT  $\Rightarrow t_{on}/t_{off} \uparrow \Rightarrow f_s \downarrow \approx 20$  KHz.

GTO  $\Rightarrow$  lowest  $f_s \downarrow \approx \underline{\underline{200-300}}$  Hz.

Other non-idealities in the switch may also be considered.

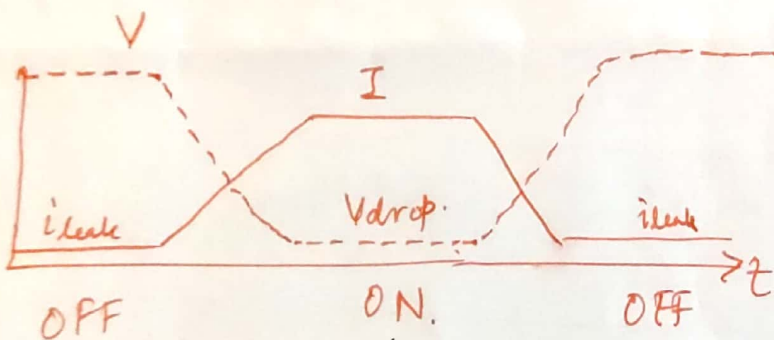- i) leakage current when OFF
- ii) Voltage drop when ON.



$$\text{Loss} = \text{Blocking} + \text{Conduction} + \text{Switching}$$

$$= (V \times i_{\text{leak}}) + (V_{\text{drop}} \times I) + ( )$$

Switching loss > Conduction loss > Blocking loss

During  $t_{on}$ :

$$\Rightarrow v(t) = V - \frac{(V - V_{\text{drop}}) \times t}{t_{on}}$$

$$i(t) = i_{\text{leak}} + \frac{(I - i_{\text{leak}}) \times t}{t_{on}}$$



During  $t_{off}$ ,

$$\Rightarrow v(t) = V_{drop} + \frac{(V - V_{drop}) \times t}{t_{off}}$$

$$i(t) = I - \frac{(I - I_{leak}) \times t}{t_{off}}$$