


HVDC Link Control Schemes:

R: CIA, CC, VDCOL


I: CEA, CB, CC, VDCOL

$\alpha \rightarrow$ delay angle


Types of Control Schemes:

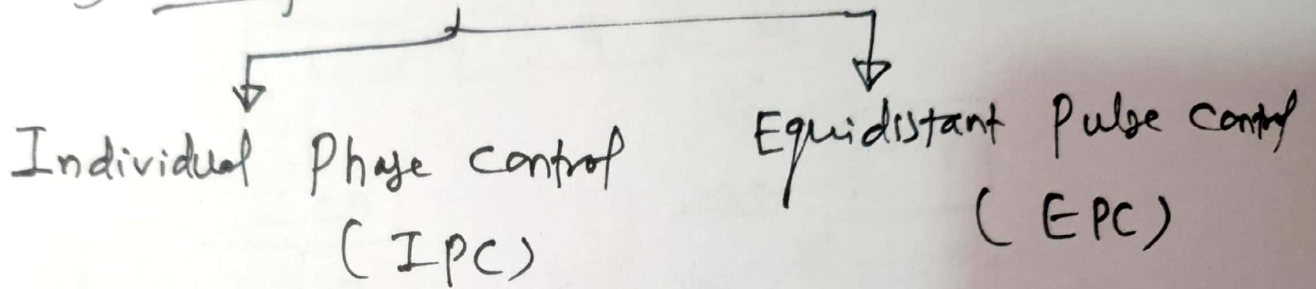


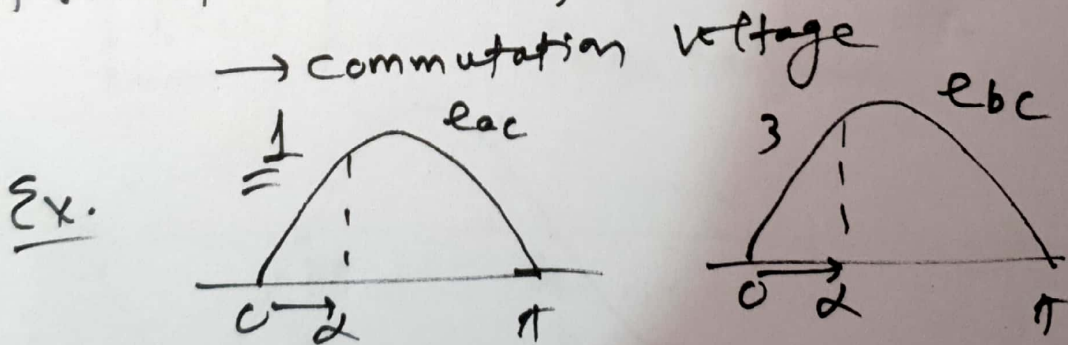
i) IPC Technique: - In this control technique the firing instant of each valve is determined individually.



Six parallel delay CKTs.

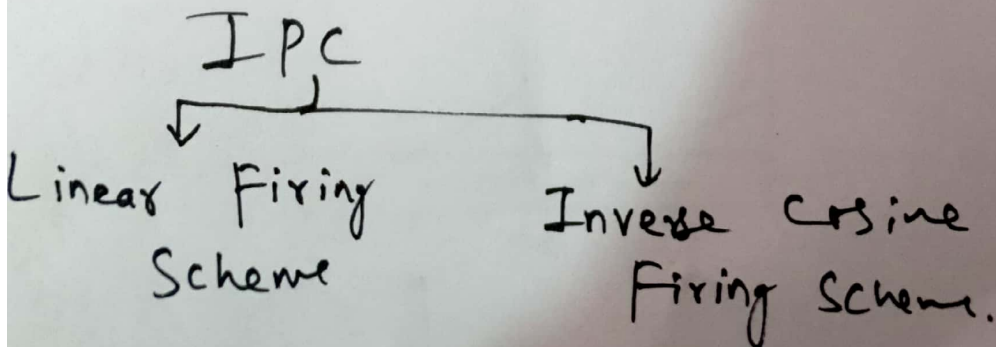

a) Linear Firing Scheme:

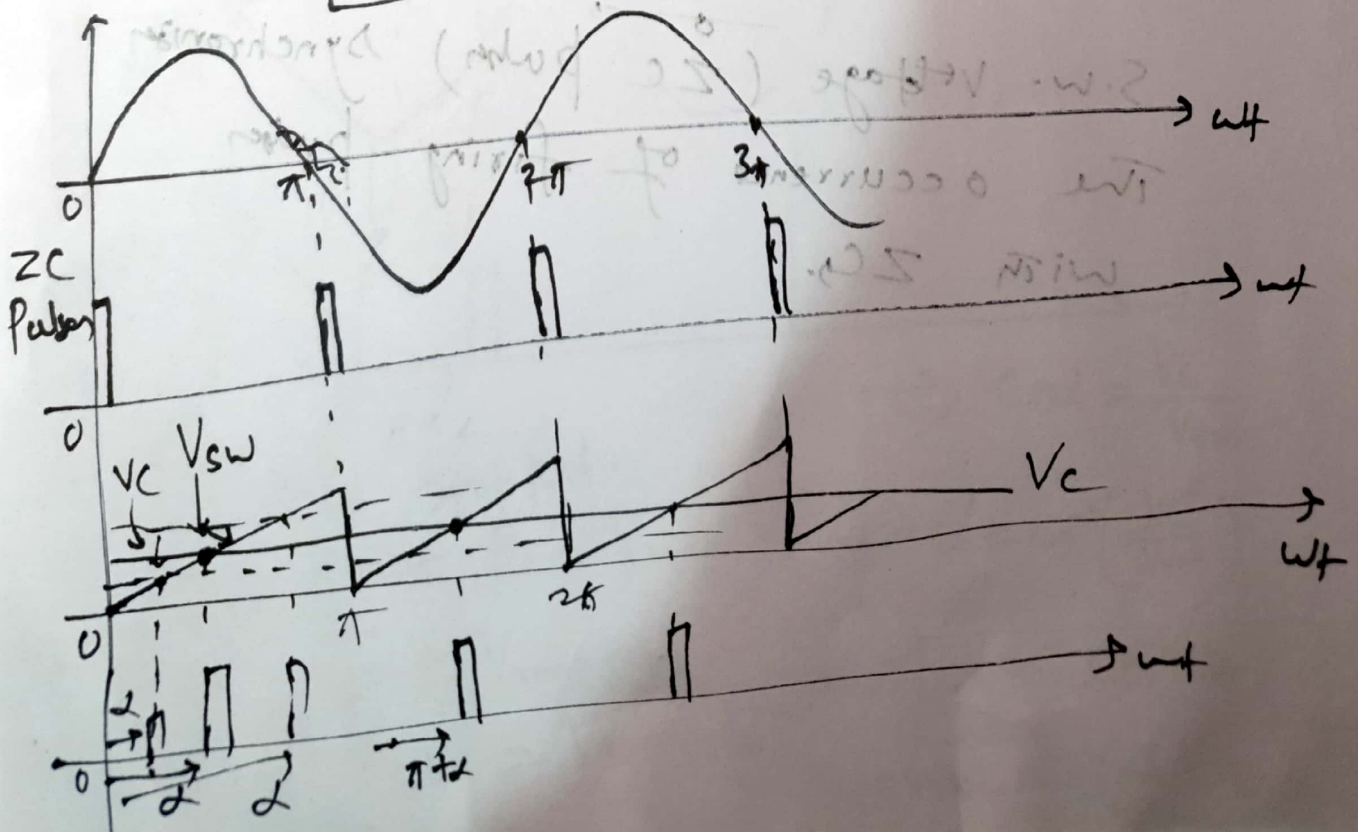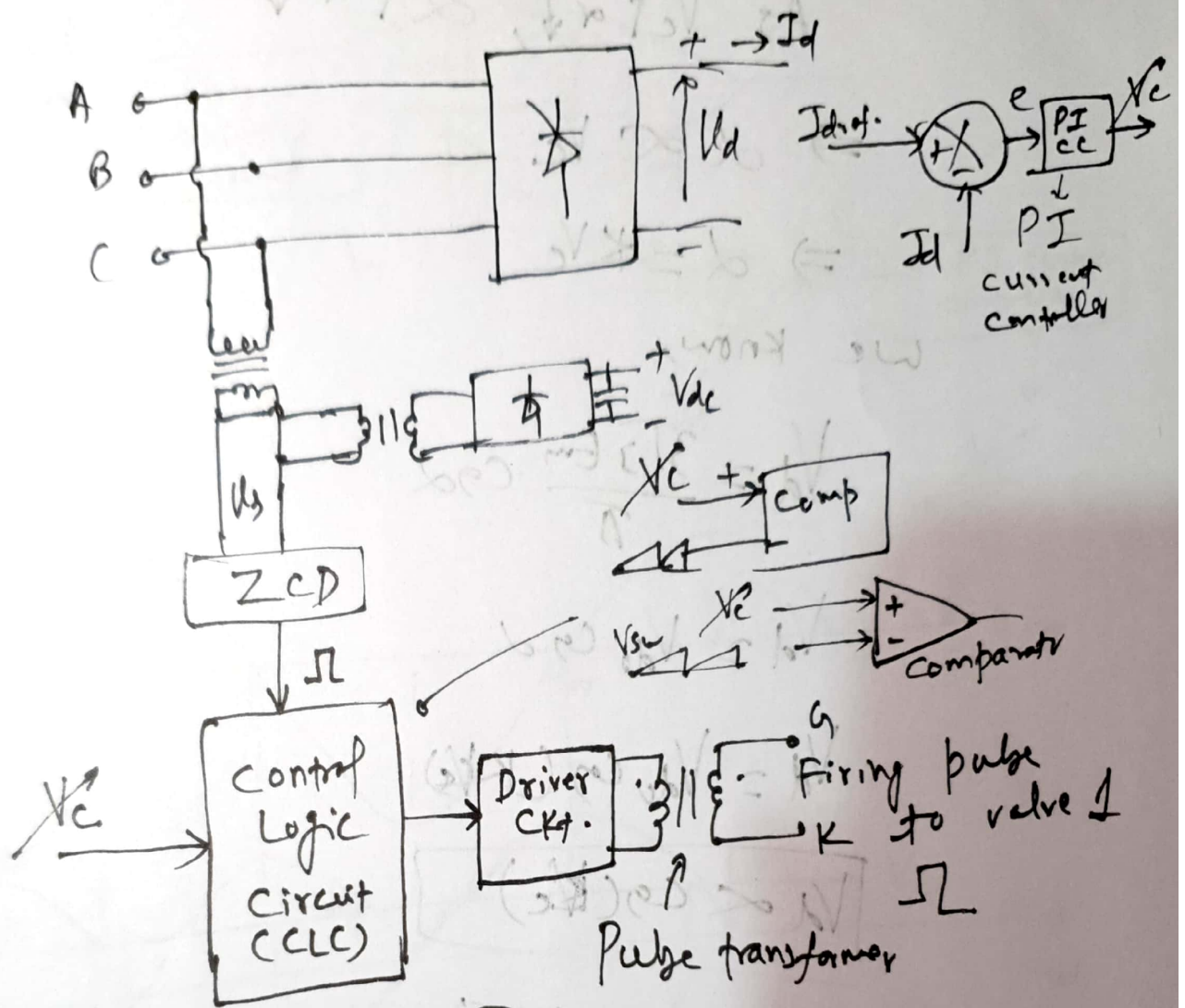

As $V_c \uparrow \alpha \downarrow$, $\alpha \uparrow \alpha \downarrow$

$\Rightarrow \alpha \propto V_c$

$\Rightarrow \alpha = K V_c$

We know,

$$V_d = \frac{3\sqrt{3} E_m}{\pi} \cos \alpha$$



$V_d = V_{d0} \cos \alpha$

$V_d = V_{d0} \cos (K V_c)$

$V_d \propto \cos (K V_c)$

S.w. voltage (ZC pulses) synchronization
 The occurrence of firing pulses
 with ZC.

b) Inverse Cosine Firing Scheme:

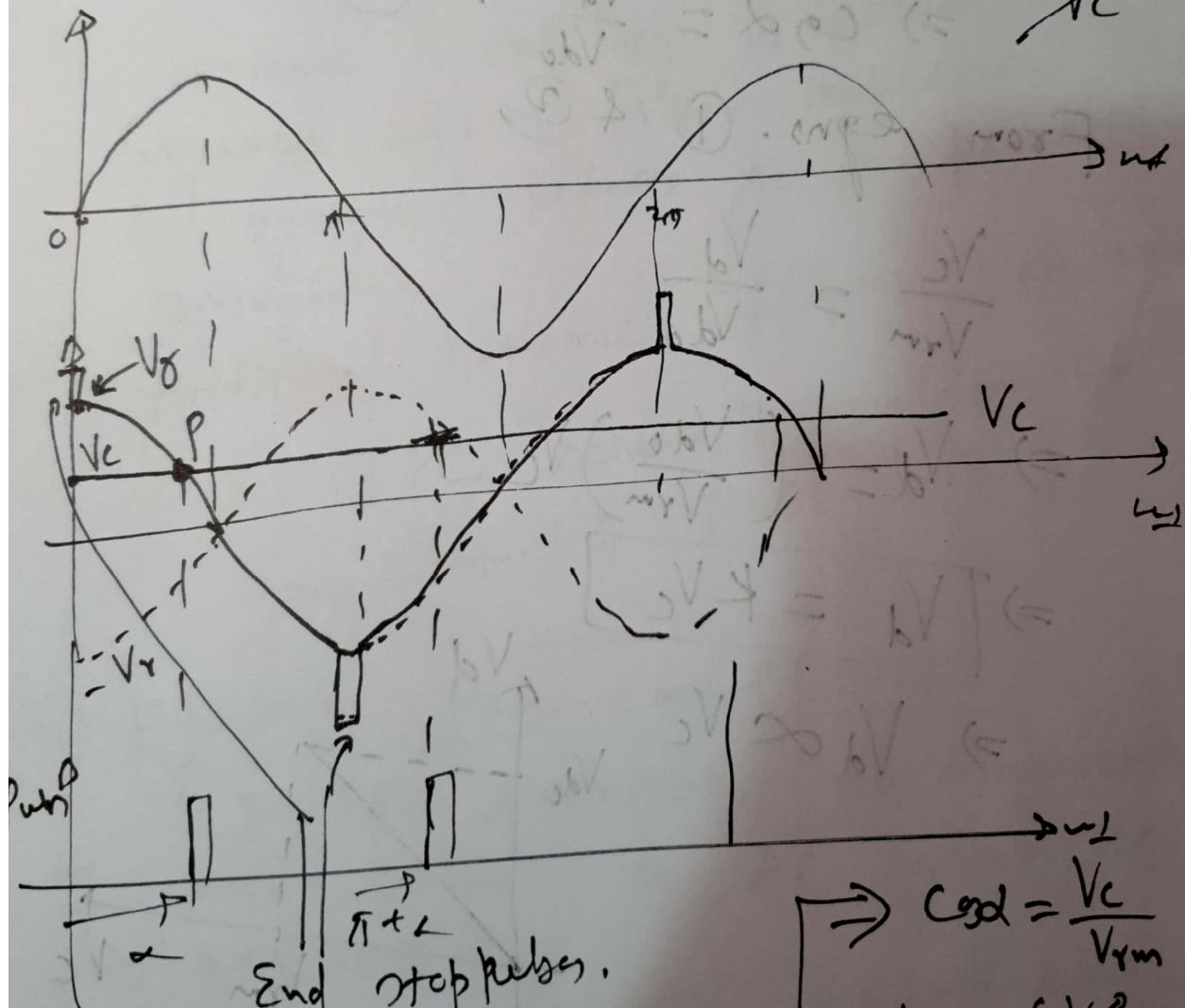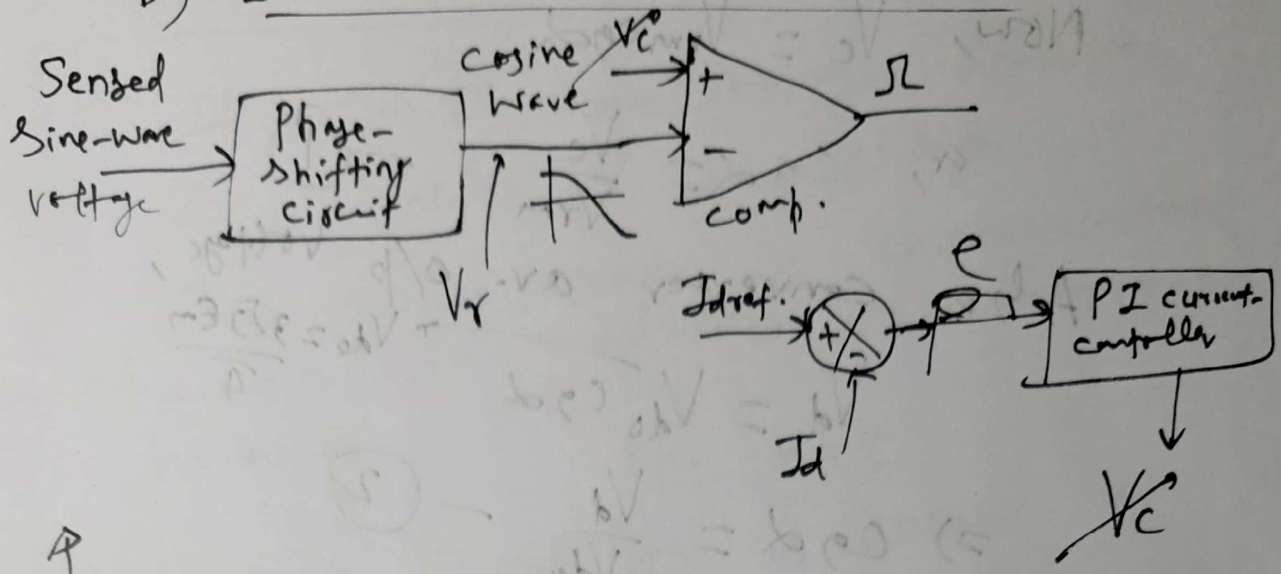

At point P, $V_r = V_c$
 $V_r = V_{rm} \cos \alpha$
 $\therefore V_c = V_{rm} \cos \alpha$

$$\Rightarrow \cos \alpha = \frac{V_c}{V_{rm}}$$

$$\therefore \alpha = \cos^{-1} \left(\frac{V_c}{V_{rm}} \right)$$

$$\Rightarrow \alpha \propto \cos^{-1}(V_c)$$

\Rightarrow Inverse Cosine firing scheme.

Now, $V_c = V_{rm} C_g \alpha$

or, $C_g \alpha = \frac{V_c}{V_{rm}}$

①

Also converter av. o/p voltage,

$V_d = V_{do} C_g \alpha$ $V_{do} = \frac{3\sqrt{3} E_m}{\pi}$

$\Rightarrow C_g \alpha = \frac{V_d}{V_{do}}$ — ②


From eqns. ① & ②,

$\frac{V_c}{V_{rm}} = \frac{V_d}{V_{do}}$

$\Rightarrow V_d = \left(\frac{V_{do}}{V_{rm}} \right) V_c$

$\Rightarrow \boxed{V_d = K V_c}$

$\Rightarrow V_d \propto V_c$

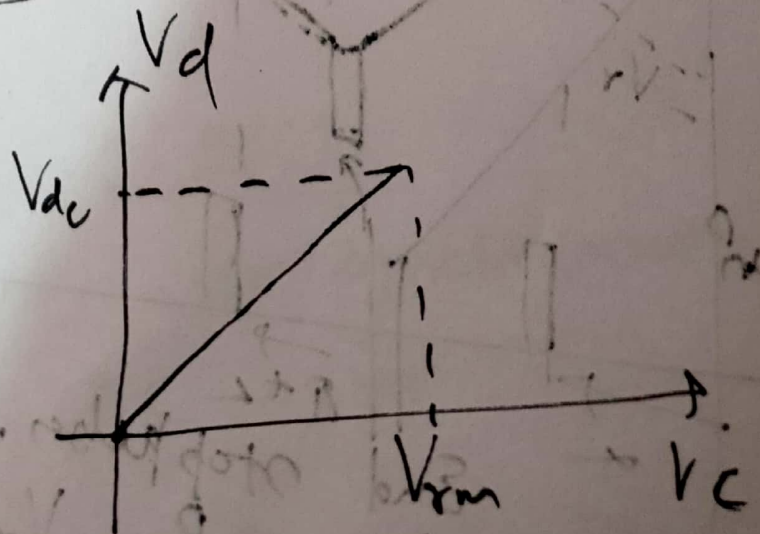

Drawbacks of IPC Scheme:

i) If, due to some voltage distortion, ZC shifts, α also changes.

This will result in uncharacteristic harmonics in addition to characteristic harmonics.

$$h = np \pm 1$$

ii) Harmonic instability is caused at frequencies where filter impedances & system impedances go in parallel resonance.

iii) Additional harmonic filters are required.

So, IPC scheme is seldom used for control of HVDC Link.


i) Equidistant Pulse control (EPC):

In EPC technique, no synchronization of control pulses with AC system (ZC) is required.

Let $\alpha_1 = 5^\circ$

$\therefore \alpha_2 = 60 + 5 = 65^\circ$

$\alpha_3 = 65 + 60 = 125^\circ \dots$

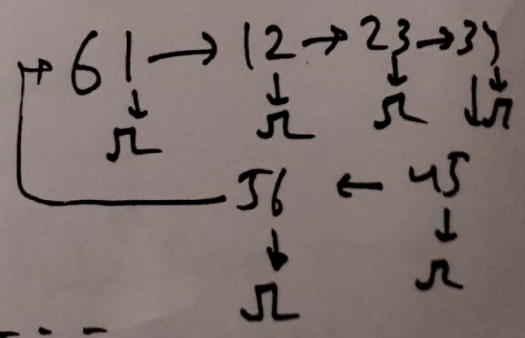


gt produces pulses at equal intervals ⁽⁵⁾
 of $\frac{1}{fp}$.

$$\omega t = \frac{2\pi}{p}$$

$$\Rightarrow t = \frac{2\pi}{\omega p} = \frac{2\pi}{2\pi f p}$$

$$\Rightarrow \boxed{t = \frac{1}{fp}} \rightarrow \text{sec.}$$

Drawback:

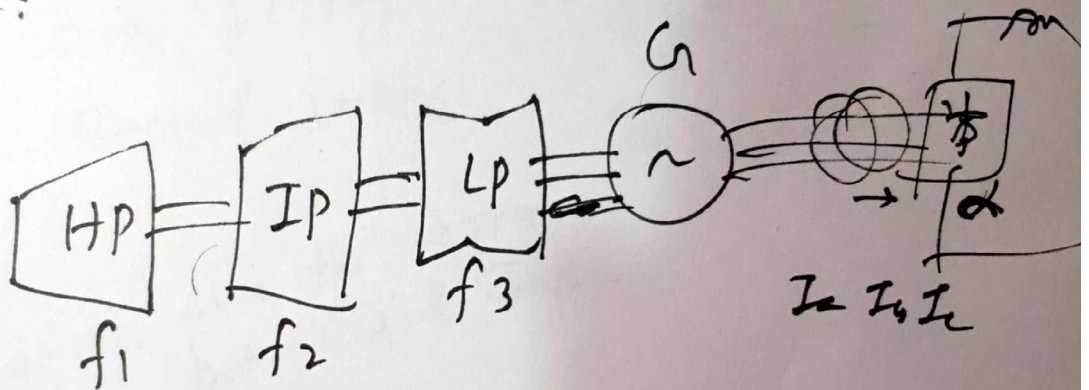


$$f_1, f_2, f_3 < 50 \text{ Hz}$$

Torsional oscillations


→ Turbine shafts → damaged.

EPC scheme produces -ive damping
 contribution to torsional oscillations.

EPC Scheme

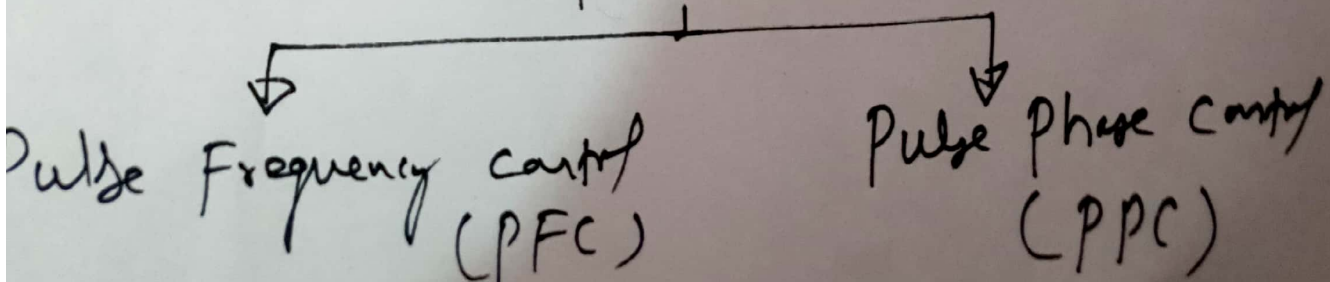




PFC Scheme:

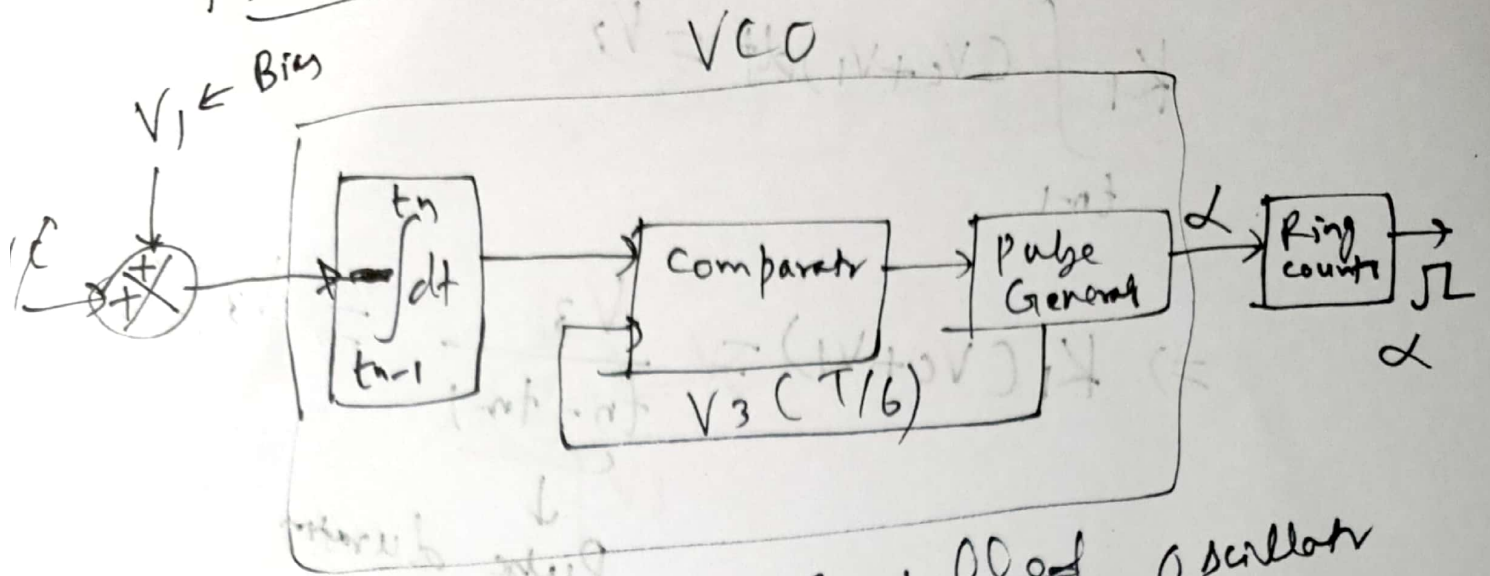

VCO: Voltage - Controlled Oscillator

V_1 : Bias voltage

V_c : Control voltage

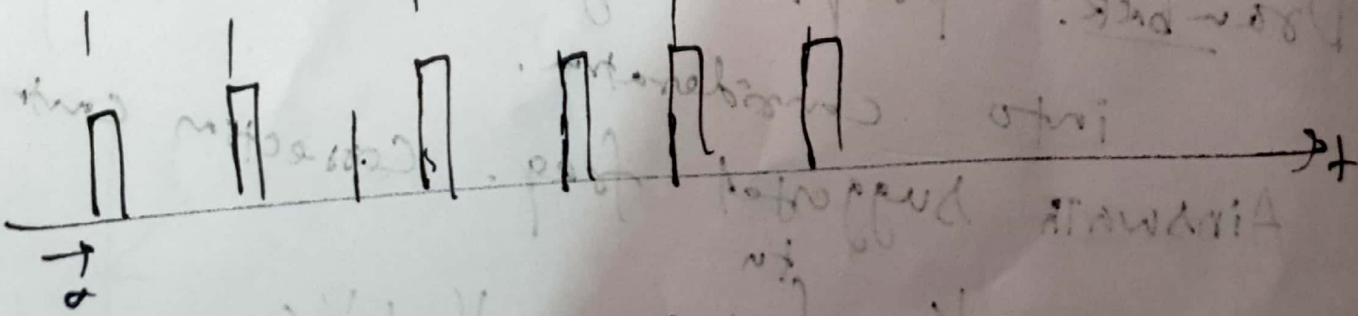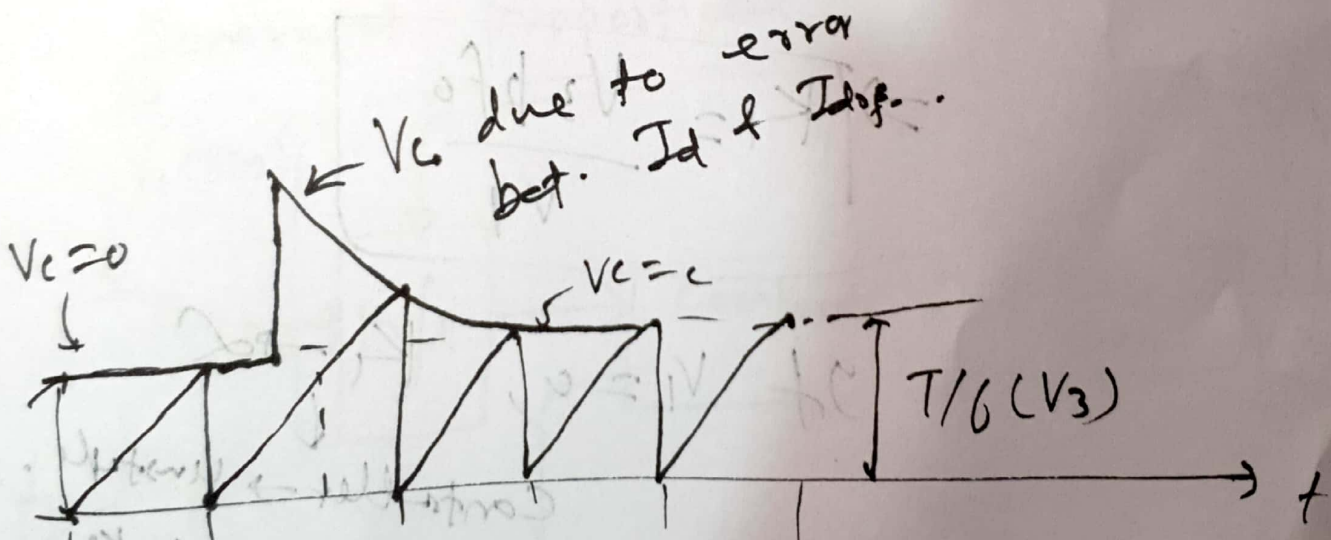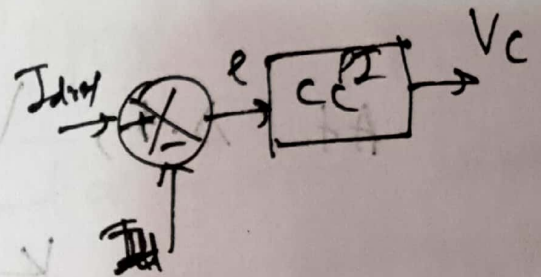

$$K_1 \int_{t_{n-1}}^{t_n} (V_c + V_1) dt = V_3$$


$$\Rightarrow K_1 (V_c + V_1) = \frac{V_3}{t_n - t_{n-1}} = V_3 b f_0$$

↓
Pulse duration

At S.S., $V_c = 0$

$$\therefore K_1 V_1 = V_3 b f_0$$
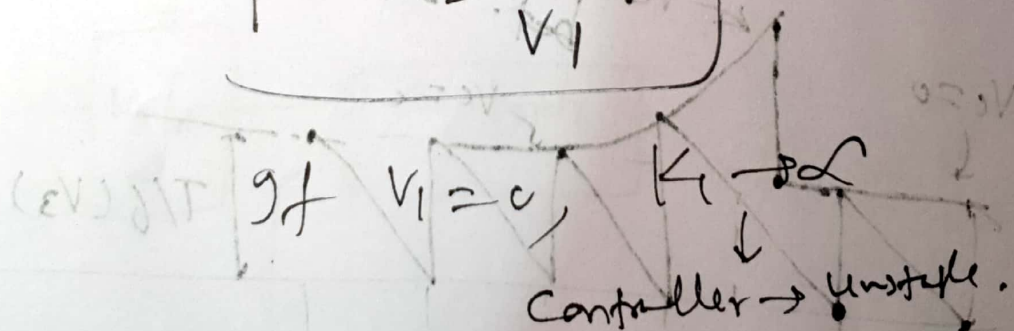
$$\Rightarrow K_1 = \frac{V_3 b f_0}{V_1}$$




Drawback: Freq. change is not taken

into consideration.

Ainsworth suggested freq. correction control,



$$K_1 \int_{t_{n-1}}^{t_n} V_1 dt = V_3 + V_c$$
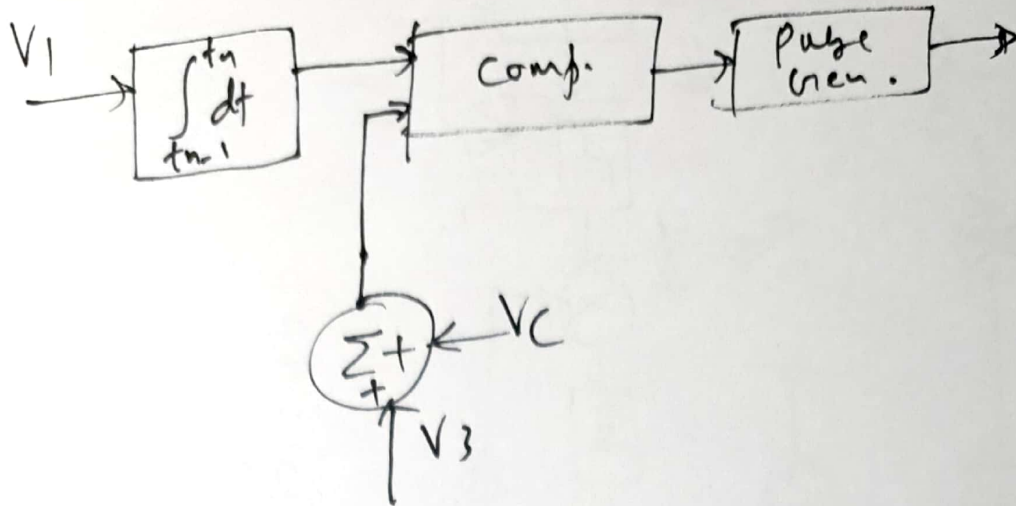
$$\Rightarrow K_1 = \frac{V_3 b f_0}{V_1}$$




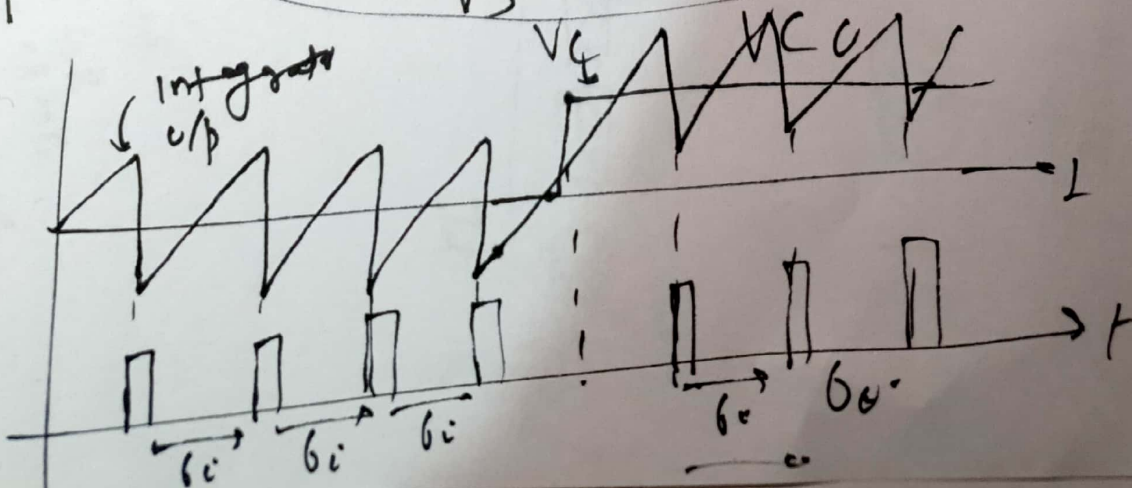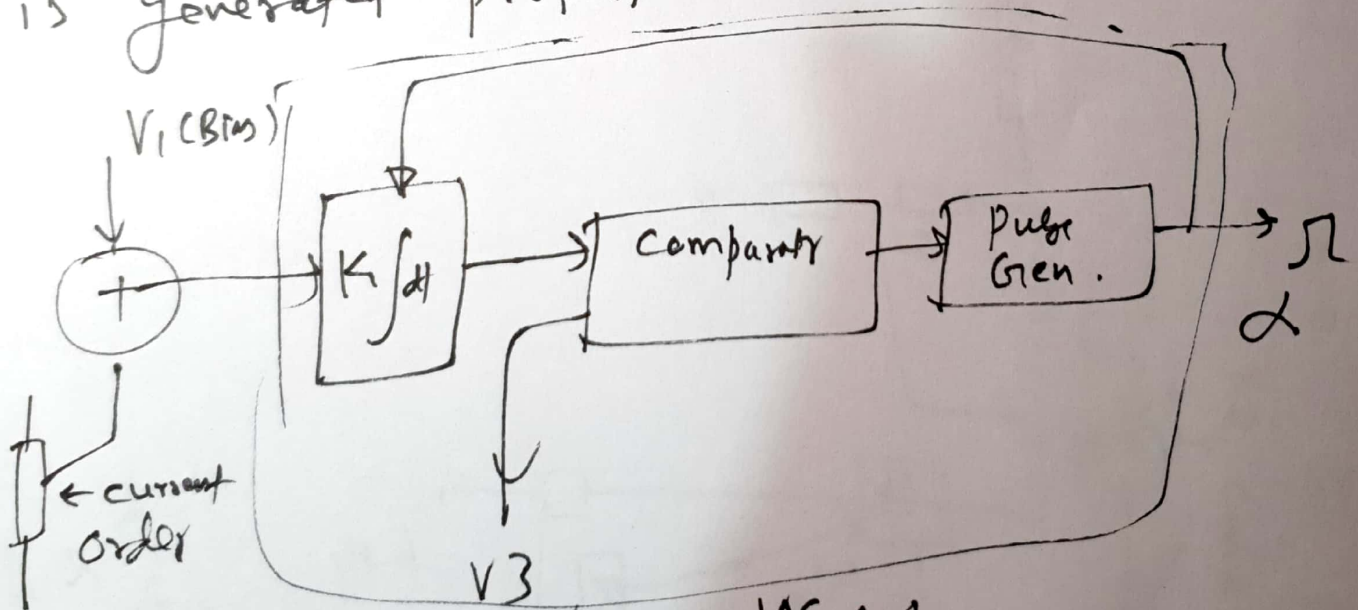b) Pulse Phase control (PPC):

A train of control or firing pulses is generated proportional to control voltage, V_c .



complete Basic Control Scheme of HVDC

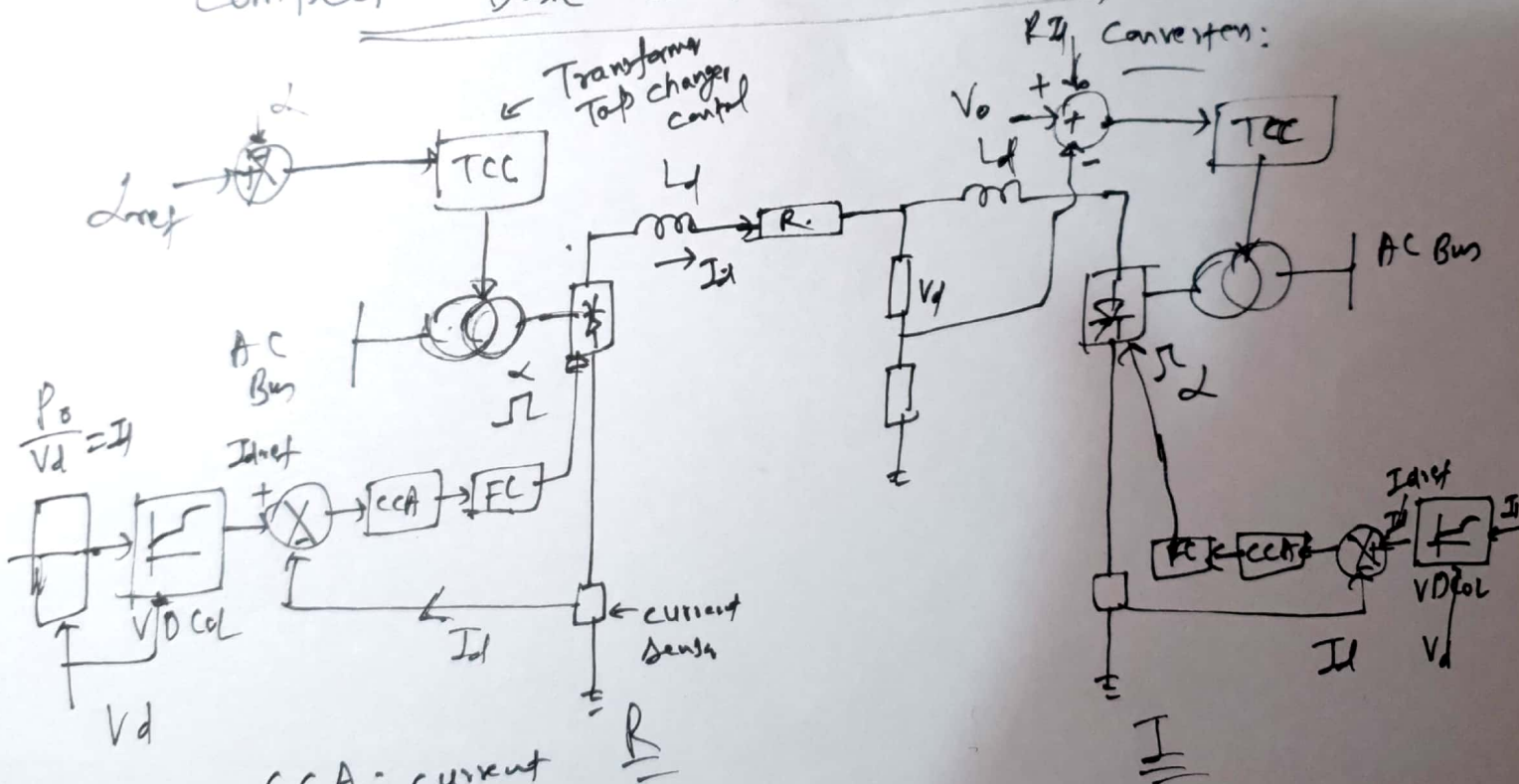

CCA: current control Amplifier

FC: Firing Ckt.

395 mB
 3.25 uB
 317.98 mB
 8 62.43 mB